

**Kathmandu University**

**Dhulikhel, Kavre**

**Department of Computer Science and Engineering**



A Mini Project Report

On

**“AIS Computer”**

**[COMP-315]**

**(For the partial fulfillment of 3<sup>rd</sup> Year/ 1<sup>st</sup> Semester in Computer Engineering)**

**Submitted by**

**Group 1**

Salina Koirala (27)

Ishar Maharjan (29)

Aron Shrestha (42)

**Submitted to**

Pankaj Dawadi

Department of Computer Science and Engineering

**Submission Date: July 8, 2021**

## **Acknowledgment**

Our mini-project would not have come this far without the invaluable contribution of the Department of Computer Science and Engineering, who gave us the platform to explore new ideas and how to proceed further on our mini-project. We would like to express our heartfelt gratitude to our teacher Mr. Pankaj Dawadi for the opportunity.

Again, we would thank all those individuals who have helped us give a tiny bit of assistance in our project.

Sincerely,

Salina Koirala (27)

Ishar Maharjan (29)

Aron Shrestha (42)

## **Abstract**

“AIS computer” is a theoretical model of a basic computer of size 32k\*22. It has a 2-bit addressing mode, 5-bit opcode, and 15-bit address. It has 22-bit registers connected to a 22-bit common bus system and uses 15-bit address lines to refer to the memory location of the system. Similarly, our system has got 9 Memory Reference Instructions, 13 Register Reference Instructions, and 6 Input/Output Instructions.

# **Table of Contents**

<b>Acknowledgment</b>	<b>i</b>
<b>Abstract</b>	<b>ii</b>
<b>Table of Contents</b>	<b>iii</b>
<b>List of Tables</b>	<b>iv</b>
<b>List of figures</b>	<b>v</b>
<b>Chapter 1: Introduction</b>	<b>1</b>
<b>Chapter 2: Design Considerations</b>	<b>2</b>
2.1 Instruction Format	2
2.2 Registers	2
2.3 Flip Flops	4
2.4 Common Bus System:	5
2.5 Types of Instructions	6
Addressing Mode Decoder	6
2.6 Instruction cycle	11
2.7 Interrupt cycle	12
2.8 Control signals	12
<b>Chapter 3: Individual Designs</b>	<b>16</b>
3.1 Registers	16
3.2 Flip Flop	21
3.3 Memory	25
3.4 ALU	26
<b>Chapter 4: Conclusion</b>	<b>29</b>

## List of Tables

1. Registers used in AIS Computer	3
2. Addressing Mode Decoder	7
3. Memory reference instruction set	10
4. Register reference instruction set	11
5. I/O instruction set	28

## List of figures

Figure 2.1: 22-bit memory word

Figure 2.2: Control Unit of AIS Computer

Figure 2.3: Direct Memory Reference Instruction Format

Figure 2.4: Indirect Memory Reference Instruction Format

Figure 2.5: Register Reference Instruction Format

Figure 2.6: Input/Output Instruction Format

Figure: Instruction cycle flowchart

Figure 3.1.1: Address Register

Figure 3.1.2: Data Register

Figure 3.1.3: Accumulator

Figure 3.1.4: Program Counter

Figure 3.1.5: Temporary Register

Figure 3.1.6: Instruction Register

Figure 3.1.7: Output Register

Figure 3.2.1: E flipflop

Figure 3.2.2: R flipflop

Figure 3.2.3: S flipflop

Figure 3.2.4: Sequence counter

Figure 3.2.5: IEN flipflop

Figure 3.2.6 FGI flip flop

Figure 3.2.7 FGO flip flop

Figure 3.3.1: Memory write

Figure 3.3.1: Memory read

Figure 3.4.1 :ALU

Figure 3.4.2 : Control for Common Bus System

## Chapter 1: Introduction

The Basic computer generally has two components, a processor and a memory. A processor is responsible for performing different operations of the system. Based on the different sets of instructions it can perform, different types of registers used, size of memory, timing and control system, interrupts, etc., different organizations of basic computers are determined.

AIS Computer,  $32K \times 22$ , has a very simple architecture compared to today's complex computers. Our computer has a 2-bit addressing mode, 5-bit opcode, and 15-bit address. It supports basic arithmetic and logic operations such as addition, subtraction, AND, OR, etc. An accumulator is used to store the output of an ALU operation. The data register is used to store data from memory before performing any operations on them. Address register and stack pointer are both used to specify memory address with the help of a common address bus. Data is transferred between registers using a common address bus. Program counter stores the next instruction to be executed, and the computer interfaces with the user using input and output registers. All the instructions are executed using the signals generated by the control unit consisting of a sequence counter and an extensive collection of logic gates.

The hardware components of AIS Computer are:

- A memory unit of 32K (32768) words with 22 bits each.
- Nine registers: AR, PC, DR, AC, IR, TR, OUTR, INPR, and SC.
- Eight flip-flops:  $I_1$ ,  $I_0$ , S, E, R, IEN, FGI, and FGO.
- A 22 -bits common bus.
- Control logic gates.
- Decoders



## Chapter 2: Design Considerations

### 2.1 Instruction Format

The instruction format of the AIS computer is as shown in the figure below:

- 2 bits addressing mode
- 5 bits opcode
- 15 bits memory address

 


Figure 2.1: 22-bit memory word

### 2.2 Registers

Registers	Bit Size	Bits
PC	15	0-14
AR	15	0-14
IR	22	0-21
TR	22	0-21
DR	22	0-21
AC	22	0-21
INPR	8	0-7
OUTR	8	0-7
SC		

Table 2.1: Registers used in AIS Computer

A brief description of registers :

- Program Counter (PC): It contains the address of the memory location where the next instruction is located. During each execution of an instruction, the value of PC is incremented by one pointing at the next instruction that needs to be executed. AIS PC is a 15-bit register.
- Address Register(AC): It holds the address of the operand in the memory. This address lets the specific operand come out from memory and go to the memory. It is 15 bits as only 15 bits are required to specify a particular address in a memory having  $2^{15}$  registers.
- Instruction Register(IR): It stores the 22-bit instruction code read from memory. Both the input and output of the instruction register come from and go to the central bus system.
- Temporary Register (TR): It stores temporary data during the working of the computer. It is of 22 bits.
- Data Register(DR): It is a 22-bit register used to store the operand read from the memory to be processed. The output of the data register is interfaced with the ALU. Any value that is to be operated must at first be transferred to the Data register.
- Accumulator (AC): Accumulator is the main register of this computer. It is 22-bit and stores the result of any operation after its completion. The input of the accumulator comes from the output of the ALU. The output of the AC goes to the common bus system as well as to ALU as the first operand, the second being the Data register.

- Input Register (INPR): It is an 8-bit register that holds the input character feed on an input device (e.g., a keyboard). Its output is connected to ALU as the value entered by the user needs to be processed with the accumulator.
- Output Register (OUTR): It is 8-bit and holds the output character that needs to be displayed to the user. Its input is connected to the central bus system.

## 2.3 Flip Flops

Flip-flop is a circuit that maintains a state until directed by input to change the state. The AIS computer has seven flip-flops. The flip flops with their uses are as follows:

- $I_0, I_1$ : These flip-flops determine the addressing mode.
- R: This flip flop determines whether you are in the instruction cycle or interrupt the cycle.
- S: It determines the start-stop state of the program.
- E: This flag determines the carry.
- IEN; This flag indicates that an interrupt has occurred.
- FGI: Indicates interrupt due to input device.
- FGO: Indicates interrupt due to output device.

## 2.4 Common Bus System:

It is a 22-bit common bus system that connects all the registers to the memory. Three selection lines control the input of the bus. The following figure is a block diagram of the common bus system of the computer.

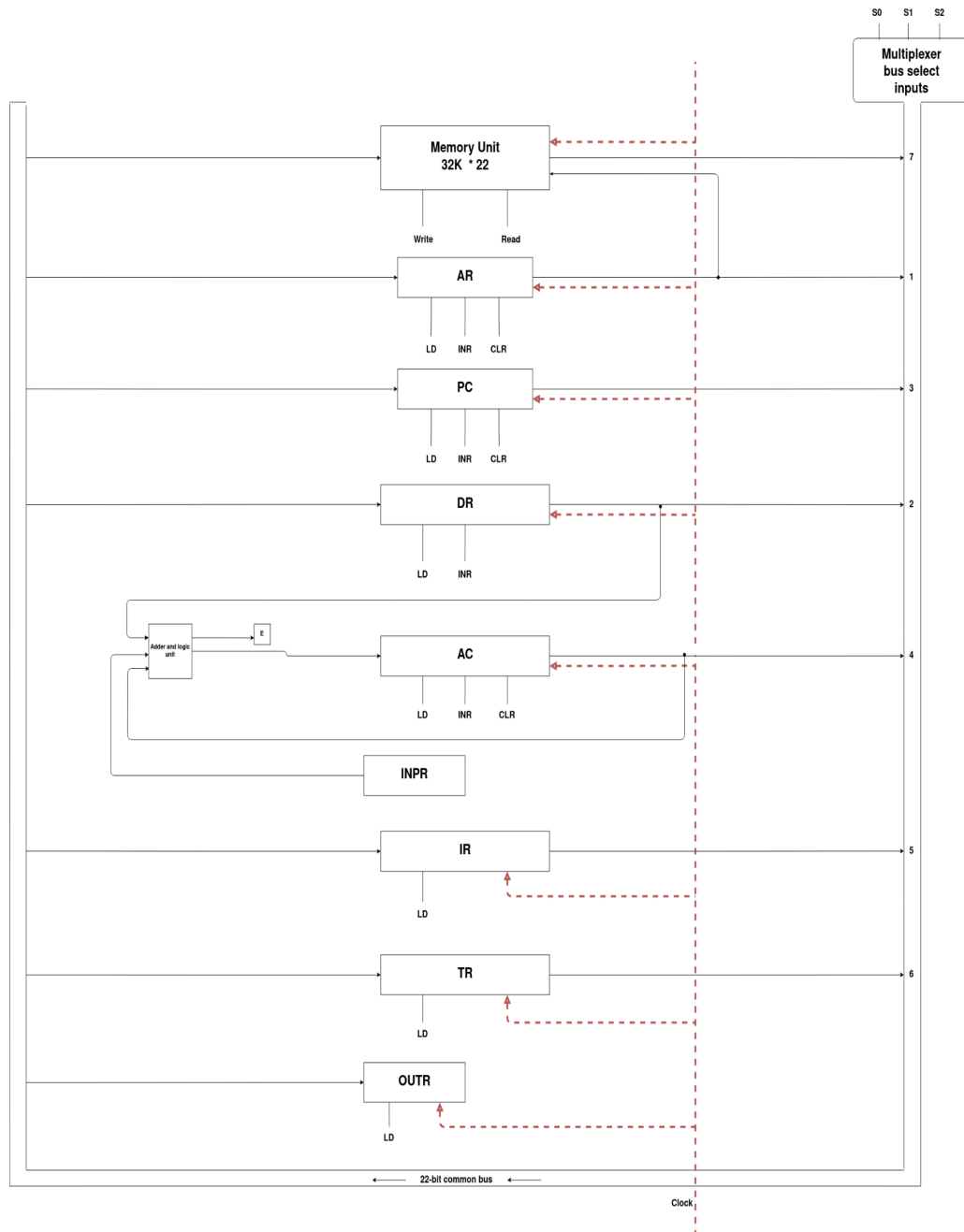


Figure 2.2: Control Unit of AIS Computer

## 2.5 Types of Instructions

The instruction code is divided into three parts, an opcode (Operation Code) that specifies the operation for that instruction and an address that specifies the registers and/or locations in memory to use for that operation. Also, it has two bits for determining addressing mode.

### Addressing Mode Decoder

$I_1I_0$	Output (Instruction Type)
00	Input/Output Instruction
01	Direct Memory Reference Instruction
10	Indirect Memory Reference Instruction
11	Register Reference Instruction

Table 2.2: Addressing Mode Decoder

These instruction codes are a set of binary numbers in the memory word, which makes the processor do a certain task. Based on the op-code, the addressing mode flag (I), three categories of instructions are MRI, RRI, and IOI.

#### 1. Memory Reference Instruction(MRI):

When the opcode (15-19 bits) is from 00000 to 01000, the instruction is recognised as an MRI. The 0-14 bits are used for the address of an operand. The 20-21 bits  $I_0I_1$  determine the addressing mode of the instruction, which can be direct or indirect when  $I_0I_1$  is 01 or 10 respectively.

 


Figure 2.3: Direct Memory Reference Instruction Format

 


Figure 2.4: Indirect Memory Reference Instruction Format

## 2. Register Reference Instructions(RRI):

Register reference instructions are recognized by the control when  $I(I_0I_1) = 11$ . The instructions use the 5 bits opcode from 01000 to 10101 of the instruction register i.e. IR(15-19) to specify the type. The rest of the bits are neglected in this case and can be used to increase the number of instructions if needed.

 


Figure 2.5: Register Reference Instruction Format

## 3. Input Output Instruction(IOI):

If the bits  $I_0I_1$  (20-21) is 00, then the instruction is input-output instruction. The type of instruction is specified by the 5 bits opcode from 10110 to 11011. Here, 0-14 bits are neglected.

 


Figure 2.6: Input/Output Instruction Format

Here, x is the hexadecimal equivalent of the binary bits.

#### Memory reference instructions

Hex Code		Symbol	Description	Opcode bits
Direct	Indirect			
100xxx - 107xxx	200xxx - 207xxx	AND	AND memory word to AC	00000
108xxx - 10Fxxx	208xxx - 20Fxxx	OR	OR memory word to AC	00001
110xxx - 117xxx	210xxx - 217xxx	ADD	Add memory word to AC	00010
118xxx - 11Fxxx	218xxx - 21Fxxx	LDA	Load memory word to AC	00011
120xxx - 127xxx	220xxx - 227xxx	STA	Store content of AC in memory	00100
128xxx - 12Fxxx	228xxx - 22Fxxx	BUN	Branch unconditionally	00101
130xxx - 137xxx	230xxx - 237xxx	BSA	Branch and save the return address	00110
138xxx - 13Fxxx	238xxx - 23Fxxx	ISZ	Increment and skip if zero	00111
140xxx - 147xxx	240xxx - 247xxx	XOR	XOR memory word to AC	01000

Table 2.3: Memory reference instruction set

## Register reference instructions

<b>Hex Code</b>	<b>Opcod e</b>	<b>Description</b>	<b>Opcode bits</b>
<b>348xxx - 34Fxxx</b>	<b>CLA</b>	<b>Clear AC</b>	<b>01001</b>
<b>350xxx - 357xxx</b>	<b>CLE</b>	<b>Clear E</b>	<b>01010</b>
<b>358xxx - 35Fxxx</b>	<b>CMA</b>	<b>Complement AC</b>	<b>01011</b>
<b>360xxx - 367xxx</b>	<b>CME</b>	<b>Complement E</b>	<b>01100</b>
<b>368xxx - 36Fxxx</b>	<b>CIR</b>	<b>Circulate right AC and E</b>	<b>01101</b>
<b>370xxx - 377xxx</b>	<b>CIL</b>	<b>Circulate right AC and E</b>	<b>01110</b>
<b>377xxx - 37Fxxx</b>	<b>INC</b>	<b>Increment AC</b>	<b>01111</b>
<b>380xxx - 387xxx</b>	<b>DEC</b>	<b>Decrement AC</b>	<b>10000</b>
<b>388xxx - 38Fxxx</b>	<b>SPA</b>	<b>Skip next instruction if AC is positive</b>	<b>10001</b>
<b>390xxx - 397xxx</b>	<b>SNA</b>	<b>Skip next instruction if AC is negative</b>	<b>10010</b>
<b>398xxx - 39Fxxx</b>	<b>SZA</b>	<b>Skip next instruction if AC is zero</b>	<b>10011</b>
<b>3A0xxx- 3A7xxx</b>	<b>SZE</b>	<b>Skip next instruction if E is zero</b>	<b>10100</b>
<b>3A8xxx- 3AFxxx</b>	<b>HLT</b>	<b>Halt Operation</b>	<b>10101</b>

Table 2.4: Register reference instructions



### Input/output instructions

Hex Code	Opco de	Description	Opcode bits
<b>0B0xxx</b> - <b>0B7xxx</b>	<b>INP</b>	<b>Input character to AC</b>	<b>10110</b>
<b>0B8xxx</b> - <b>0BFxxx</b>	<b>OUT</b>	<b>Output character from AC</b>	<b>10111</b>
<b>0C0xxx</b> - <b>0C7xxx</b>	<b>SKI</b>	<b>Skip on the input flag</b>	<b>11000</b>
<b>0C8xxx</b> - <b>0CFxxx</b>	<b>SKO</b>	<b>Skip on output flag</b>	<b>11001</b>
<b>0D0xxx</b> - <b>0D7xxx</b>	<b>ION</b>	<b>Interrupt on</b>	<b>11010</b>
<b>0D8xxx</b> - <b>0DFxxx</b>	<b>IOF</b>	<b>Interrupt off</b>	<b>11011</b>

Table 2.5: I/O instruction set

## 2.6 Instruction cycle

The instructions in the memory need to be executed. Until a stop instruction is encountered, the instructions are executed serially. Every instruction goes through different processes (cycles) to be executed, which is called the instruction cycle as a whole. It is mainly divided into three parts: Fetch, Decode and Execute.

1. Fetch: In this cycle, the content of the PC is transferred to AR. then, the memory content in the address AR is loaded into the instruction register (IR). Also, the PC is incremented by 1 to point to the next instruction for later. RTLs for this cycle is given below:

$$R'T_0: AR \leftarrow PC$$

$$R'T_1: IR \leftarrow M[AR], PC \leftarrow PC + 1$$

2. Decode: During this cycle, the 20-21 bits of IR is loaded into  $I_1I_0$  flip flops. The bits from 15-19 are decoded and the type of instruction is determined which can be MRI, RRI or I/O instruction. Remaining 0-14 bits are loaded into AR. The RTLs for this cycle is given below:

$$R'T_2: I_1I_0 \leftarrow IR(20-21),$$

$$A_0...A_8, B_0...B_7, C_1...C_6 \leftarrow IR(15-19), AR \leftarrow IR(0-14)$$

$$I_0'I_1T_3: AR \leftarrow M[AR]$$

3. Execute: This cycle is where the actual execution of instruction occurs accordingly. The complete set of RTI and control functions for different types of instructions are listed later in the report.

## 2.7 Interrupt cycle

During the execution cycle of each instruction, the computer keeps checking for an interrupt to occur. If any output or input devices are triggered, it is said that an interrupt has occurred and the IEN flag is set to 1, then a special cycle known as interrupt cycle is executed. When any input interrupt occurs, the FGI flag is set to 1 and when any output interrupt occurs, the FGO flag is set to 1. During the interrupt cycle, the return address is saved in a specific memory address. Then, the program branched to the pre-contained input/output program in the memory and after that, it returns back to the program where it was before interruption. Until the interrupt cycle is executed fully, no further interrupts are allowed to occur. RTLs for this cycle is given below:

$T_0'T_1'T_2'(IEN)(FGO+FGI): R \leftarrow 1$   
 $RT_0 : AR \leftarrow 0, TR \leftarrow PC$   
 $RT_1 : M[AR] \leftarrow TR, PC \leftarrow 0$   
 $RT_2 : PC \leftarrow PC+1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$

## 2.8 Control signals

The complete set control signals of all the instructions are given below:

### Fetch:

$R'T_0: AR \leftarrow PC$   
 $R'T_1: IR \leftarrow M[AR], PC \leftarrow PC + 1$

### Decode:

$R'T_2: I_0I_1 \leftarrow IR(20-21), A_0...A_8, B_0...B_7, C_1...C_6 \leftarrow IR(15-19),$   
 $AR \leftarrow IR(0-14)$   
 $I_0'I_1T_3: AR \leftarrow M[AR]$

### Interrupt:

$T_0'T_1'T_2'(IEN)(FGO+FGI): R \leftarrow 1$   
 $RT_0 : AR \leftarrow 0, TR \leftarrow PC$   
 $RT_1 : M[AR] \leftarrow TR, PC \leftarrow 0$   
 $RT_2 : PC \leftarrow PC+1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$

**Execute:**

### Memory reference instructions

**AND:**

A0 T4:  $DR \leftarrow M[AR]$   
A0 T5:  $AC \leftarrow AC \wedge DR, SC \leftarrow 0$

**OR:**

A1 T4:  $DR \leftarrow M[AR]$   
A1 T5:  $AC \leftarrow AC \vee DR, SC \leftarrow 0$

**ADD:**

A2 T4:  $DR \leftarrow M[AR]$   
A2 T5:  $AC \leftarrow AC + DR, E \leftarrow Cout, SC \leftarrow 0$

**LDA:**

A3 T4:  $DR \leftarrow M[AR]$   
A3 T5:  $AC \leftarrow DR, SC \leftarrow 0$

**STA:**

A4 T4:  $M[AR] \leftarrow AC, SC \leftarrow 0$

**BUN:** Branch Unconditionally

A5 T4:  $PC \leftarrow AR, SC \leftarrow 0$

**BSA:** Branch anA Save Return Address

A6 T4:  $M[AR] \leftarrow PC, AR \leftarrow AR + 1$   
A6 T5:  $PC \leftarrow AR, SC \leftarrow 0$

**ISZ:** Increment anA Skip-if-Zero

A7 T4:  $DR \leftarrow M[AR]$   
A7 T5:  $DR \leftarrow DR + 1$   
A7 T6:  $M[AR] \leftarrow DR, \text{if } (DR = 0) \text{ then } (PC \leftarrow PC + 1),$   
 $SC \leftarrow 0$

**XOR:** Exclusive OR

A8 T4:  $DR \leftarrow M[AR]$   
A8 T5:  $AC \leftarrow AC \oplus AR, SC \leftarrow 0$

### Register reference instructions

$R = I_0 I_1 T_3$

$B_i$  (specifies the type of RRI)

R:  $SC \leftarrow 0$

**CLA:**

$rB_0: AC \leftarrow 0$

**CLE:**  
 $rB_1: E \leftarrow 0$   
**CMA:**  
 $rB_2: AC \leftarrow AC'$   
**CME:**  
 $rB_3: E \leftarrow E'$   
**CIR:**  
 $rB_4: AC \leftarrow shr\ AC, AC(21) \leftarrow E, E \leftarrow AC(0)$   
**CIL:**  
 $rB_5: AC \leftarrow shl\ AC, AC(0) \leftarrow E, E \leftarrow AC(21)$   
**INC:**  
 $rB_6: AC \leftarrow AC + 1$   
**DEC:**  
 $rB_7: AC \leftarrow AC - 1$   
**SPA:**  
 $rB_8: \text{If } (AC(21) = 0) \text{ then } (PC \leftarrow PC + 1)$   
**SNA:**  
 $rB_9: \text{If } (AC(21) = 1) \text{ then } (PC \leftarrow PC + 1)$   
**SZA:**  
 $rB_A: \text{If } (AC = 0) \text{ then } (Pc \leftarrow Pc + 1)$   
**SZE:**  
 $rB_B: \text{If } (E = 0) \text{ then } (PC \leftarrow PC + 1)$   
**HLT:**  
 $rB_C: S \leftarrow 0$

### Input output instructions

$P = I_1' I_0' T_3$   
 $C_i$  (specifies the type of I/O I)

**INP:**  
 $pC_1: AC(0-7) \leftarrow INPR, FGI \leftarrow 0$   
**OUT:**  
 $pC_2: OUTR \leftarrow AC(0-7), FGO \leftarrow 0$   
**SKI:**  
 $pC_3: \text{if } (FGI = 1) \text{ then } (PC \leftarrow PC + 1)$   
**SKO:**  
 $pC_4: \text{if } (FGO = 1) \text{ then } (PC \leftarrow PC + 1)$   
**ION:**  
 $pC_5: IEN \leftarrow 0$   
**IOF:**  
 $pC_6: IEN \leftarrow 0$

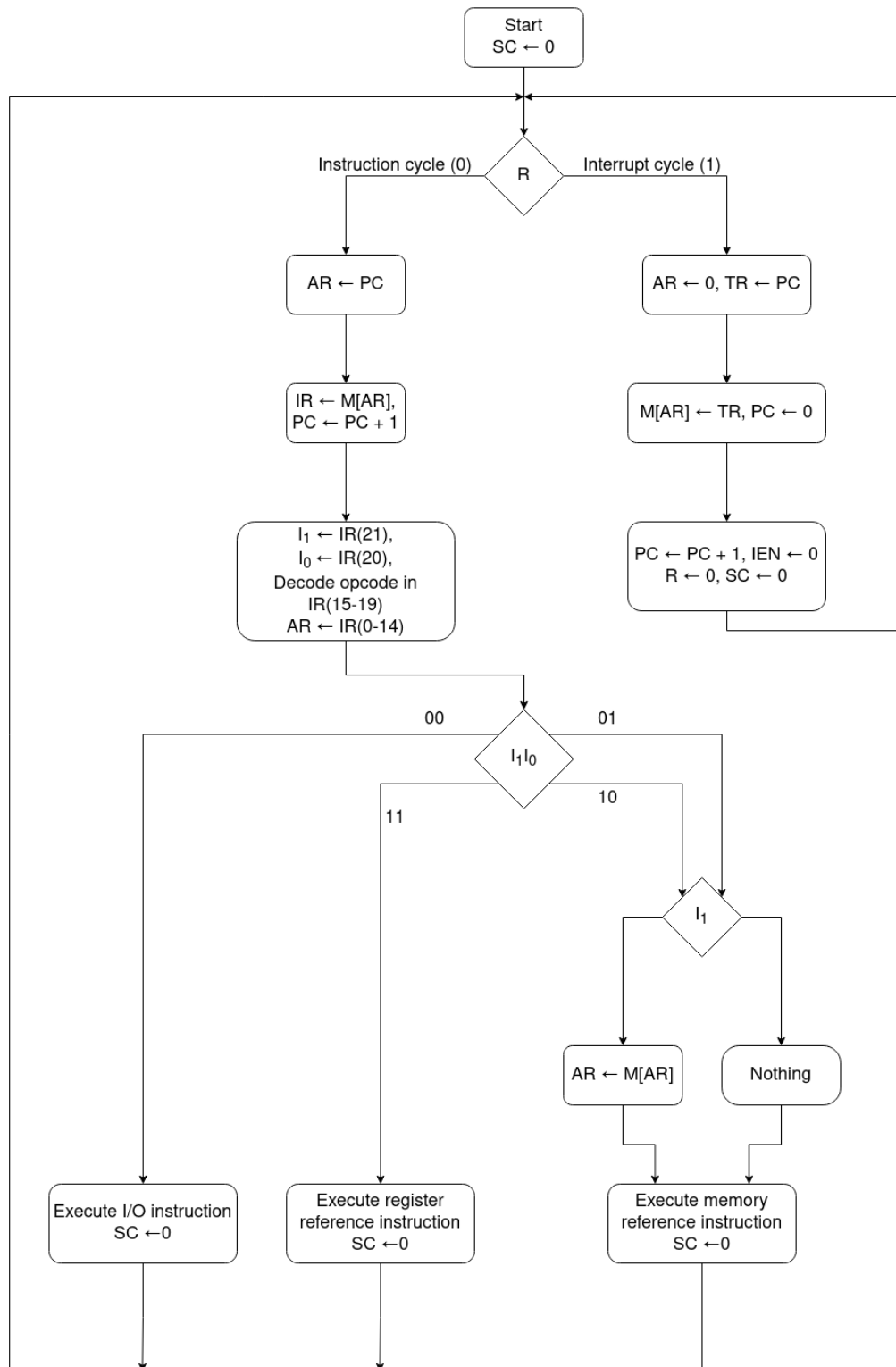


Figure 2.7: Instruction cycle flowchart

## Chapter 3: Individual Designs

### 3.1 Registers

#### 1) Address Register

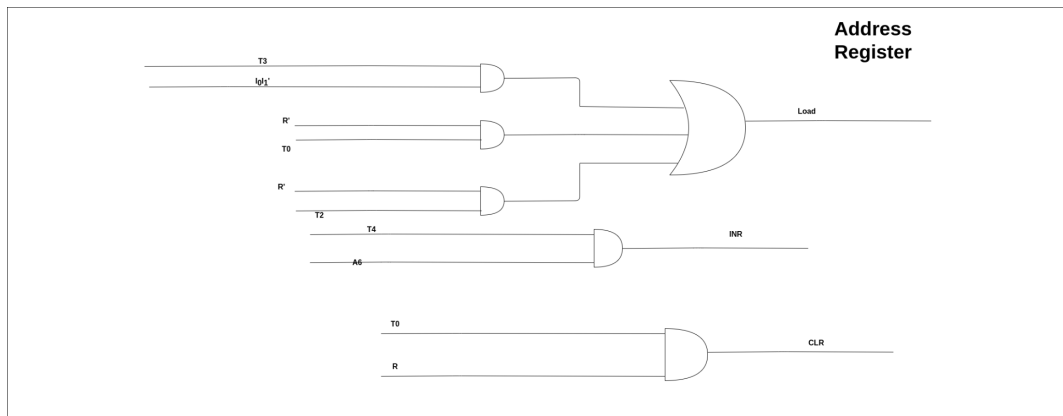


Fig 3.1.1: Address Register

$$\begin{aligned}\text{CLR} &= RT_0 \\ \text{INCR} &= A_6T_4 \\ \text{LOAD} &= R'T_0 + R'T_2 + T_3 \cdot I_0 \cdot I_1'\end{aligned}$$

## 2)Data Register

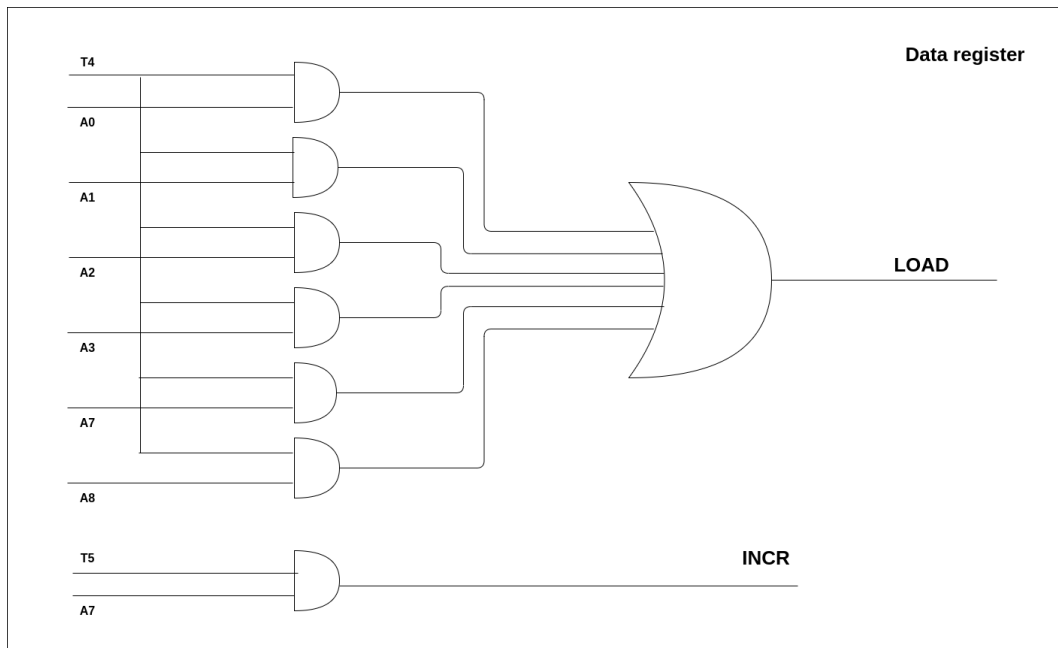


Fig 3.1.2: Data Register

$$\text{LOAD} = (A_0 + A_1 + A_2 + A_3 + A_7 + A_8) \cdot T_4$$

$$\text{INCR} = T_5 \cdot A_7$$



### 3)Accumulator

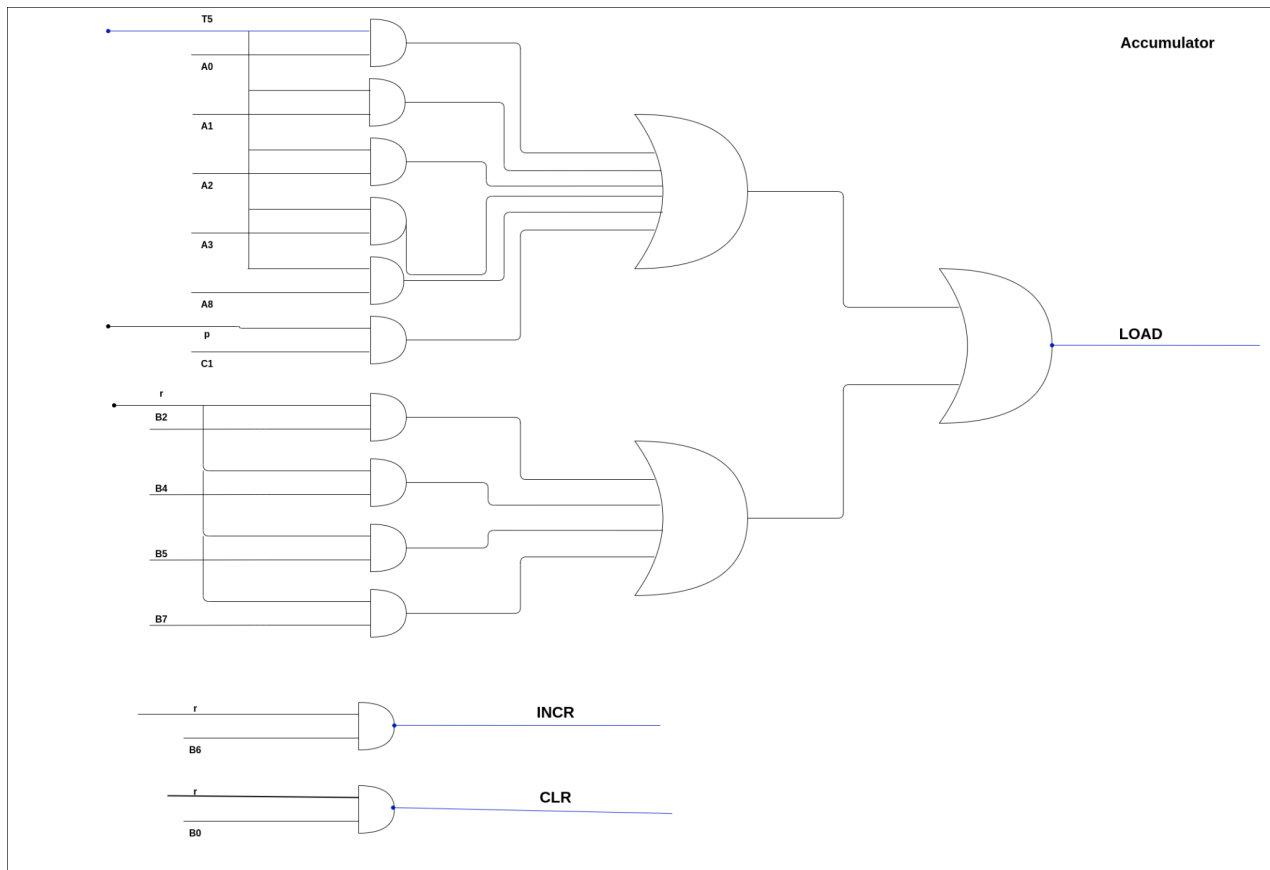


Fig 3.1..3: Accumulator

**LOAD:**  $(A_0 + A_1 + A_2 + A_3 + A_8).T_5 + rB_2 + rB_4 + rB_5 + rB_7 + pC_1$

**INCR:**  $rB_6$

**CLR :**  $rB_0$

#### 4)Program Counter

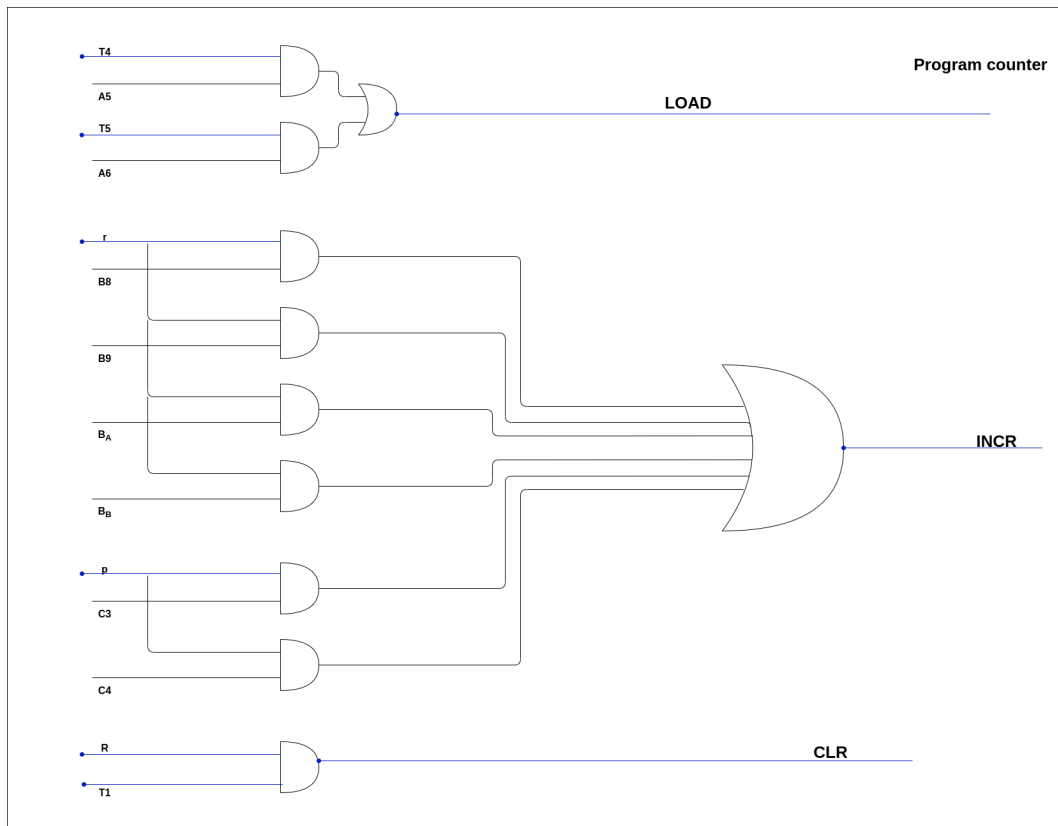


Fig 3.1.4: Program Counter

Load:  $A_5T_4 + A_6T_5$

Increment =  $rB_8 + rB_9$

#### 5)Temporary Register

 


Fig 3.1.5: Temporary Register

LOAD =  $R.T_0$

## 6) Instruction Register

 


Fig 3.1.6: Instruction Register

$$\text{LOAD} = R' \cdot T_1$$

## 7) Output Register

 


Fig 3.1.7: Output Register

$$\text{LOAD} = T_3 \cdot C_1$$

## 3.2 Flip Flop

1)E

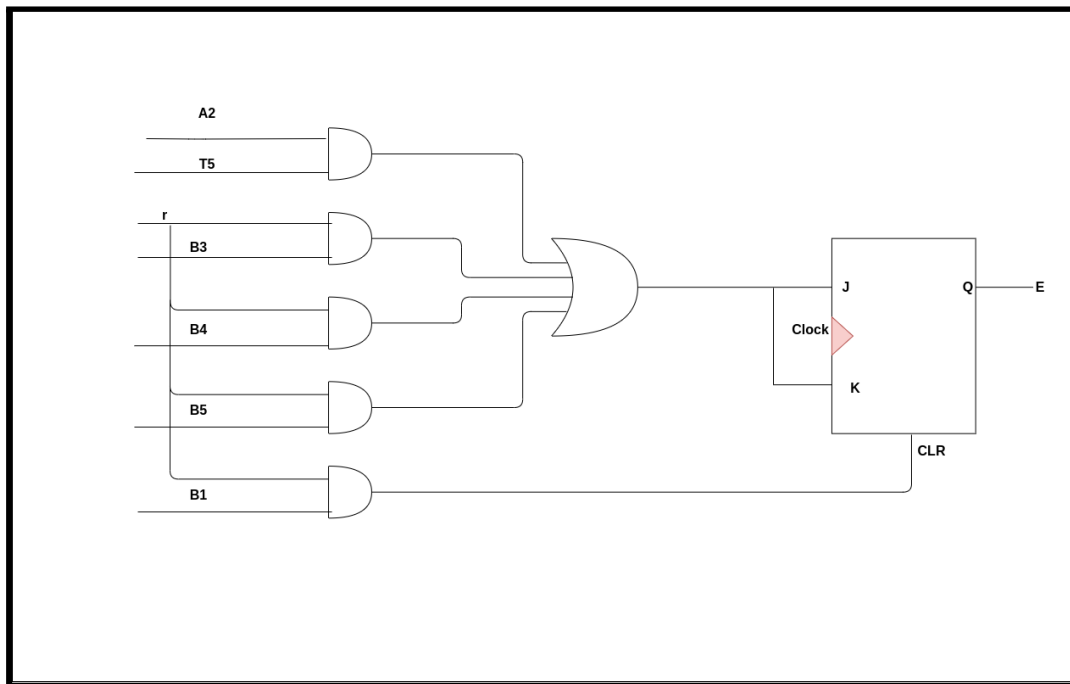


Fig 3.2.1: E flipflop

LOAD:  $rB3 + rB4 + rB5 + A2T5$   
CLEAR :  $rB1$

2)R

 


Fig 3.2.2: R flip flop

SET :  $T_0'T_1'T_2'.IEN.(FGO+FGI)$   
 RESET:  $RT_2$

3)S

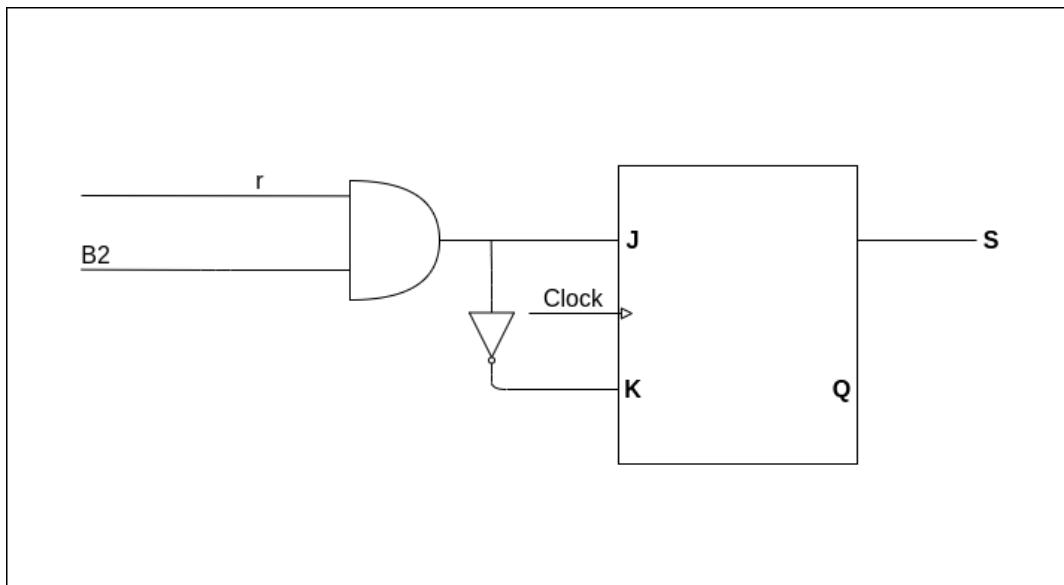


Fig 3.2.3: S flip flop

SET:  $rB_2$   
 RESET:  $SET'$

4)SC

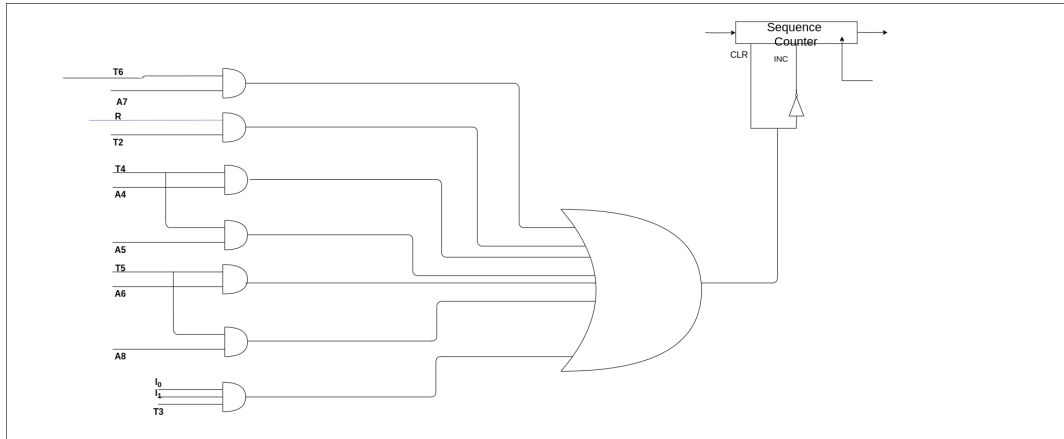


Fig 3.2.4: Sequence counter

CLR:  $T_6A_7 + RT_2 + T_4A_4 + T_4A_5 + T_5A_6 + T_5A_8 + I_0I_1T_3$   
 INC: CLR'

5) IEN

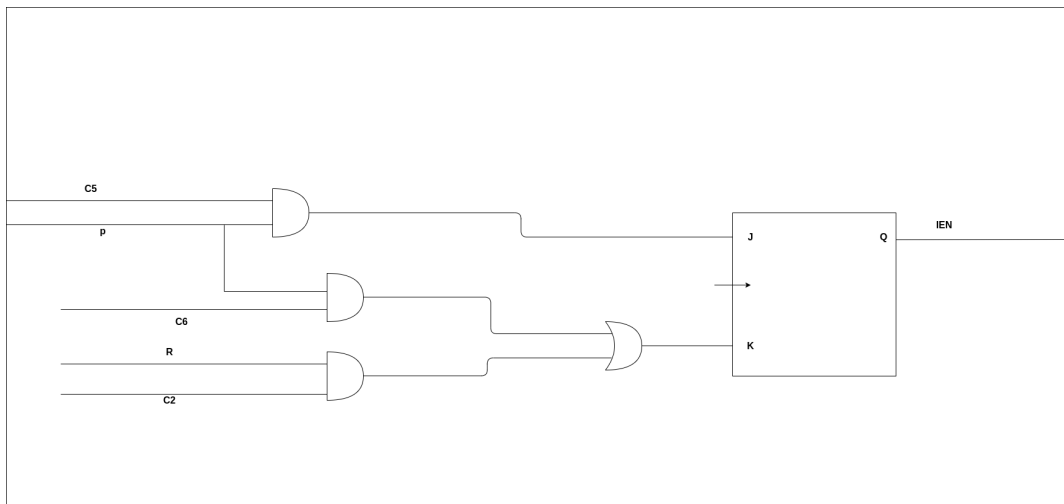


Fig 3.2.5: IEN flip flop

SET:  $pC_5$   
 RESET:  $pC_6 + RC_2$

6)FGI

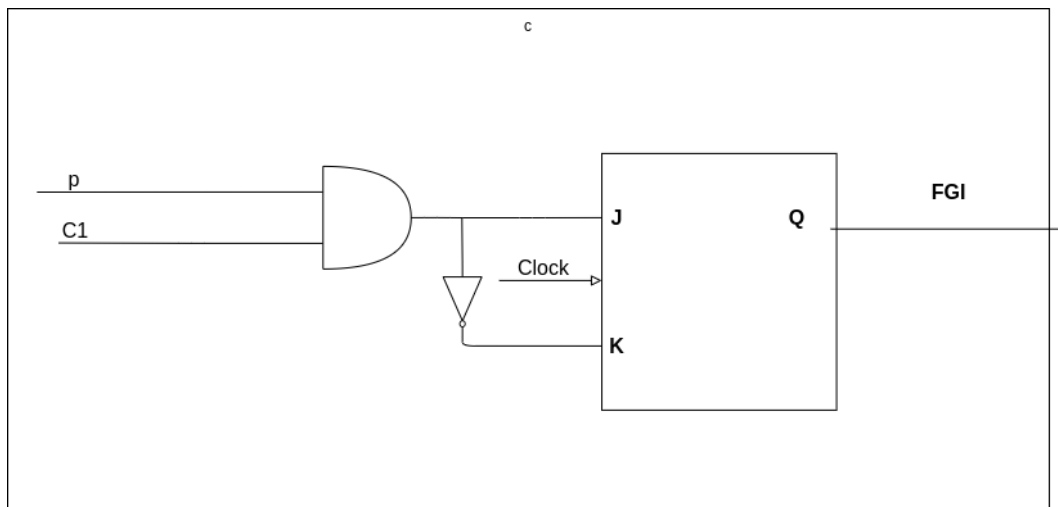


Fig 3.2.6 FGI flip flop

SET:  $pC_1$

7)FGO

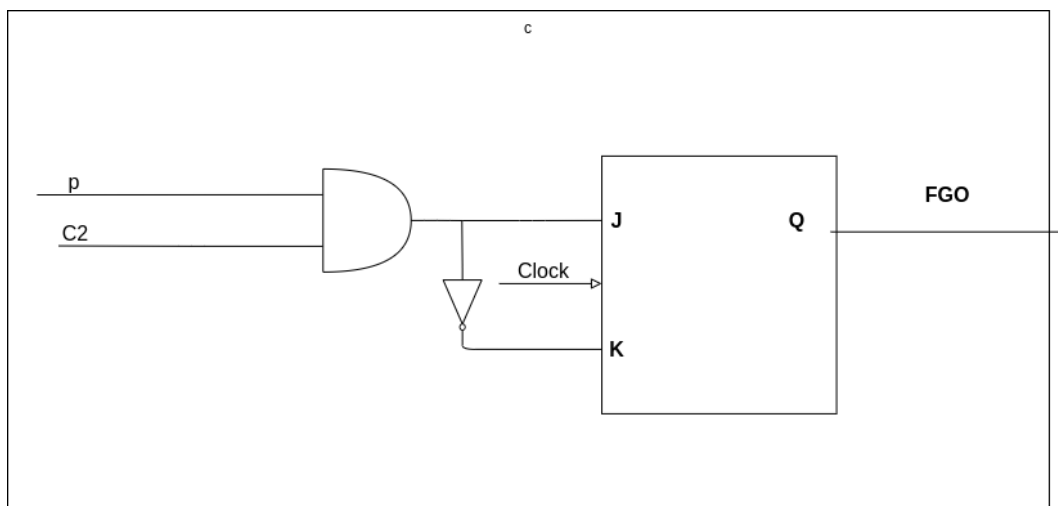


Fig 3.2.7 FGO flip flop

SET:  $pC_2$

### 3.3 Memory

#### 1) Memory write

 


Fig 3.3.1: Memory write

Write:  $A_6T_4 + A_7T_6 + RT_1$

#### 2) Memory read

 


Fig 3.3.1: Memory read

Read:  $T_3I_1'I_0 + R'T_1 + (A_0 + A_1 + A_2 + A_3 + A_7 + A_8).T_4$



### 3.4 ALU

As the name suggests, this unit performs all the arithmetic and logical calculations in the computer. Its output is directly connected to the input of the accumulator and therefore is of 15 bits in the computer design. Its inputs are connected to the outputs of the Data Register, Accumulator and the Input Register. The solution obtained from the calculation in the ALU is sent to the Accumulator, so it is from here that the output goes to the bus to its destination (i.e, Memory or the OUTR). A detailed design of a bit of the ALU is given below.

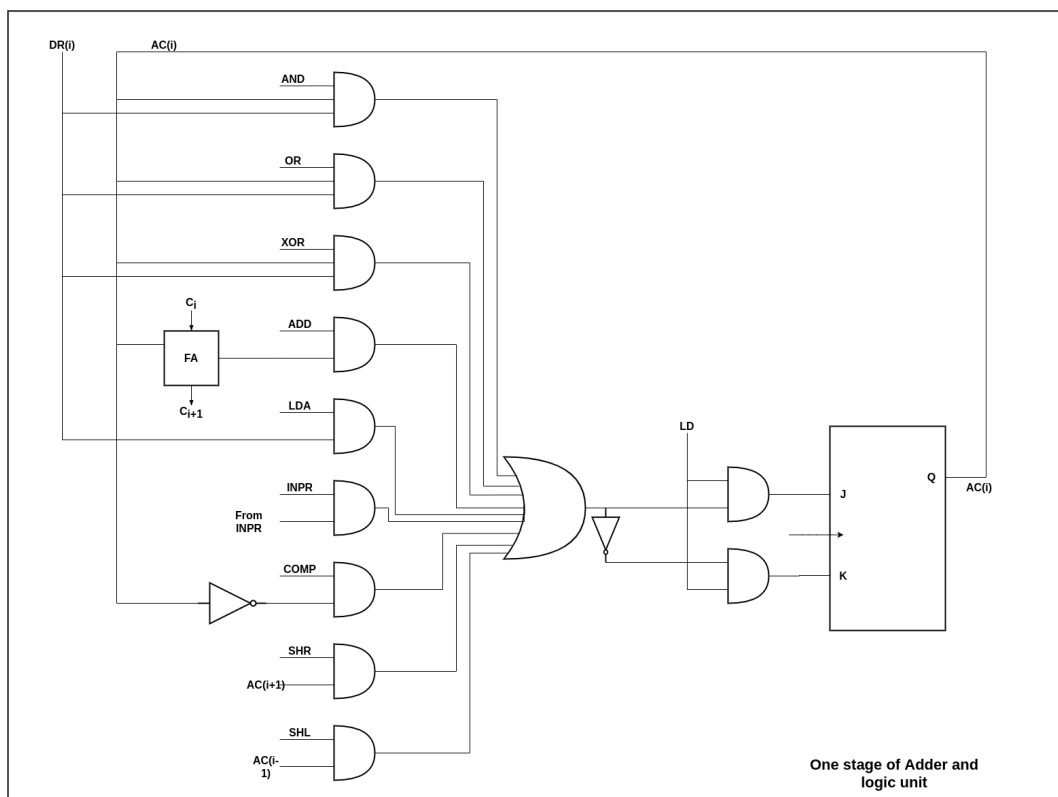


Fig 3.4.1 :ALU

## Control of common bus

Inputs							Outputs			Register selected
X1	X2	X3	X4	X5	X6	X7	S2	S1	S0	
0	0	0	0	0	0	0	0	0	0	None
1	0	0	0	0	0	0	0	0	1	AR
0	1	0	0	0	0	0	0	1	0	DR
0	0	1	0	0	0	0	0	1	1	PC
0	0	0	1	0	0	0	1	0	0	AC
0	0	0	0	1	0	0	1	0	1	IR
0	0	0	0	0	1	0	1	1	0	TR
0	0	0	0	0	0	1	1	1	1	Memory

Table 3.1: Decoder for control of common bus

$$S0 = X1 + X3 + X5 + X7$$

$$S1 = X2 + X3 + X6 + X7$$

$$S2 = X4 + X5 + X6 + X7$$

$$X1 = A5.T4 + A6.T5$$

$$X2 = A3.T5$$

$$X3 = R'.T0 + R.T0 + A6.T4$$

$$X4 = A4.T4$$

$$X5 = R'.T2$$

$$X6 = R.T1$$

$$X7 = T3.I0.I1' + R'.T1 + (A0 + A1 + A2 + A3 + A7 + A8).T4$$

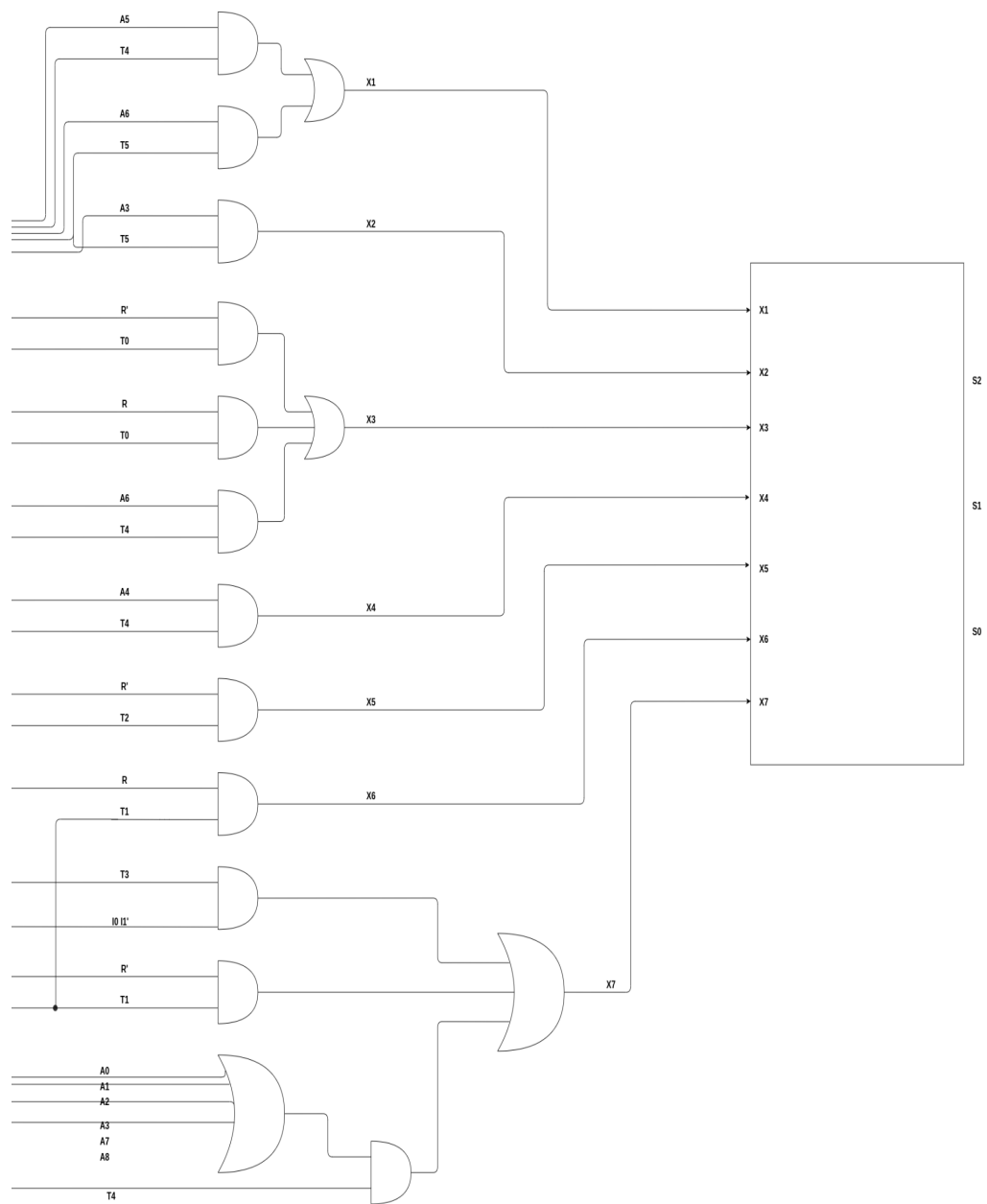


Fig 3.4.2:Control for Common Bus System

## **Chapter 4: Conclusion**

We learned the architecture of basic computers from this project. By the end of the project we got the insight of how registers , flip flops are used in basic computer and various machine level instruction. Although the computer we design is very minimal and simple it's not for commercial use . However we learned the basics of how computers are designed which is the basis for all computers.